

VHDL Lab Day3

Multiplexer

MULTIPLEXER

- A multiplexer (or **mux**) is a common digital circuit used to mix a lot of signals into just one.
- If we want multiple sources of data to share a single common data line, we have to use a multiplexer to run them into that line.
- Every multiplexer has at least one select line. (2^n inputs requires n select lines), which is used to select which input signal gets relayed to the output.
- In a 2-to-1 multiplexer, there's just one select line, 2 inputs and 1 output.
- Think of a mux as a “digital switch”. The select line is the throw on the switch, it chooses which of the many inputs get to be the output.

2:1 MUX (Dataflow):

entity mux_2_1_dataflow is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

Sel : in STD_LOGIC;

Y : out STD_LOGIC);


end mux_2_1_dataflow;

architecture Dataflow of mux_2_1_dataflow is

begin

Y<=A when Sel='0' else B;

end Dataflow;

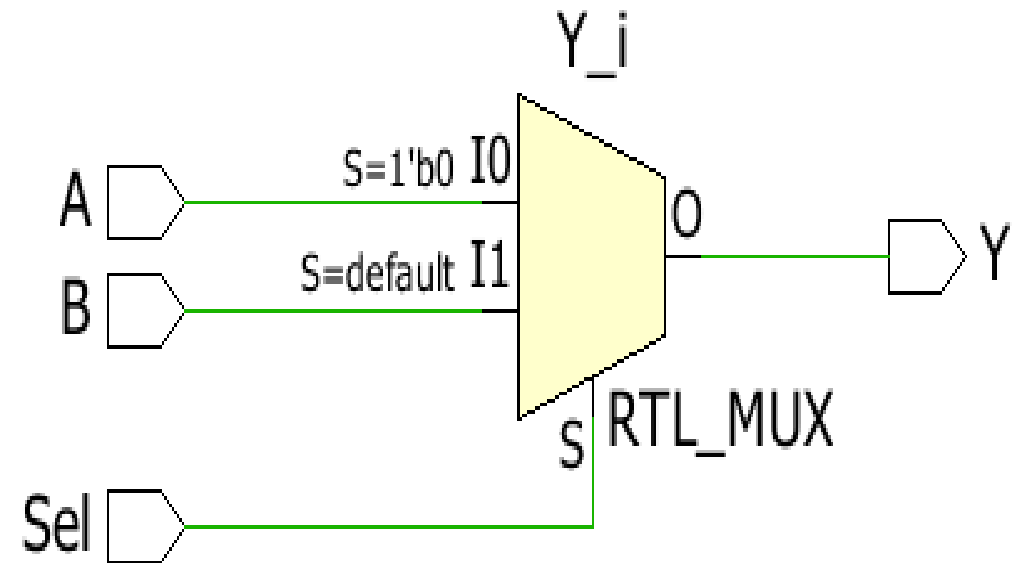

2:1 MUX (Behavioral):

architecture Behavioral of mux_2_1_behavioral is

begin

 process(A,B,Sel)

 begin

 if(Sel='0')then

 Y<=A;

 else

 Y<=B;

 end if;

 end process;

end Behavioral;

4:1 MUX (Dataflow):

VHDL code:

entity mux_4_1_dataflow is

Port (ip : in STD_LOGIC_VECTOR (3 downto 0);

s : in STD_LOGIC_VECTOR (1 downto 0);

y : out STD_LOGIC);

end mux_4_1_dataflow;

architecture Dataflow of mux_4_1_dataflow is

begin


y<=ip(0) when s="00" else

ip(1) when s="01" else

ip(2) when s="10" else

ip(3);

end Dataflow;

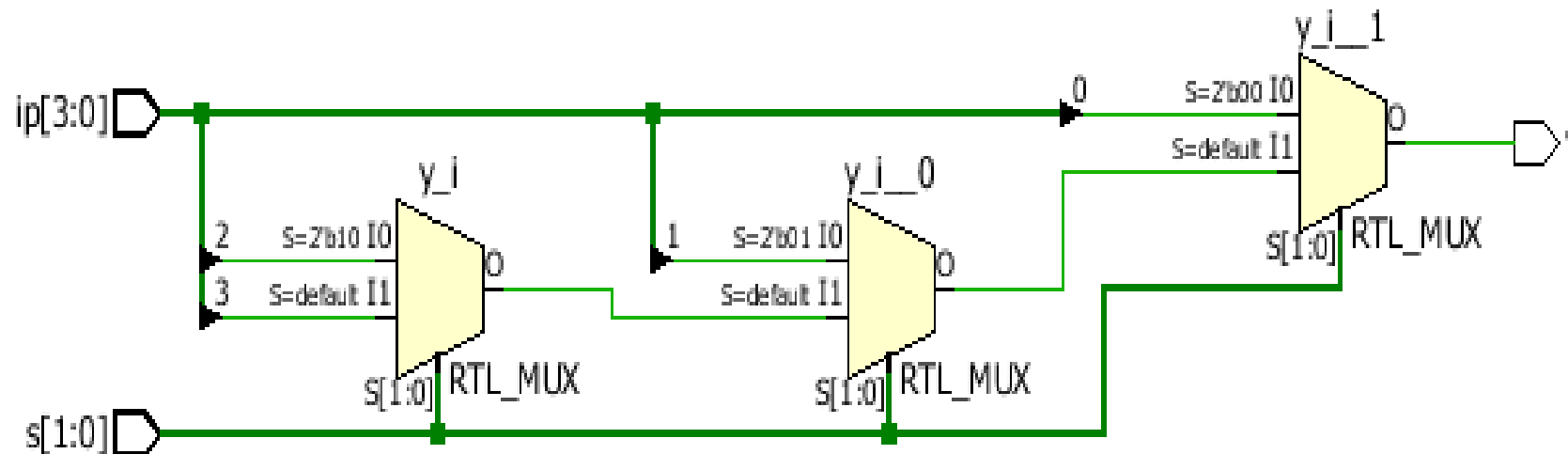

4:1 MUX (Behavioral):

VHDL code:

entity mux_4_1_behavioral is

Port (ip : in STD_LOGIC_VECTOR (3 downto 0);


s : in STD_LOGIC_VECTOR (1 downto 0);

y : out STD_LOGIC);

end mux_4_1_behavioral;

architecture Behavioral of mux_4_1_behavioral is

begin

 

process(ip,s)

begin

case s is

when "00" =>

y<=ip(0);

when "01" =>

y<=ip(1);

when "10" =>

y<=ip(2);

when "11" =>

y<=ip(3);

when others=>NULL;

end case;

end process;

end Behavioral;

TBW Code:

```
entity mux_4_1_behavioral_tb is
```

```
--  Port ( );
```

```
end mux_4_1_behavioral_tb;
```

```
architecture Behavioral of mux_4_1_behavioral_tb is
```

```
component mux_4_1_behavioral is
```

```
    Port ( ip : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          s : in STD_LOGIC_VECTOR (1 downto 0);
```

```
          y : out STD_LOGIC);
```

```
end component;
```

```
signal ip1 : STD_LOGIC_VECTOR (3 downto 0) := "0101";
```

```
signal s1 : STD_LOGIC_VECTOR (1 downto 0) := "00";
```

```
signal y1 : STD_LOGIC;
```

```
begin
```

```
    uut: mux_4_1_behavioral port map (ip=>ip1, s=>s1, y=>y1);
```

```
    stim_proc: process
```

```
    begin
```

```
        wait for 100ns;
```

```
        s1 <= "00";
```

```
        wait for 100ns;
```

```
        s1 <= "01";
```

```
        wait for 100ns;
```

```
        s1 <= "10";
```

```
        wait for 100ns;
```

```
        s1 <= "11";
```

```
        wait;
```

```
    end process;
```

```
end Behavioral;
```

3:8 Decoder (Dataflow):

VHDL code:

entity decoder_3_8_dataflow is

Port (ip : in STD_LOGIC_VECTOR (2 downto 0);

op : out STD_LOGIC_VECTOR (7 downto 0));

end decoder_3_8_dataflow;

architecture Dataflow of decoder_3_8_dataflow is

begin

op(0) <= '1' when ip="000" else '0';

op(1) <= '1' when ip="001" else '0';

op(2) <= '1' when ip="010" else '0';

op(3) <= '1' when ip="011" else '0';

op(4) <= '1' when ip="100" else '0';

op(5) <= '1' when ip="101" else '0';

op(6) <= '1' when ip="110" else '0';

op(7) <= '1' when ip="111" else '0';

end Dataflow;

Comparator 4 Bit (Dataflow):

VHDL code:

entity comparator_4 is

Port (A : in STD_LOGIC_VECTOR (3 downto 0);

B : in STD_LOGIC_VECTOR (3 downto 0);

eq : out STD_LOGIC;

gt : out STD_LOGIC;

lt : out STD_LOGIC);

end comparator_4;

architecture Dataflow of comparator_4 is

begin


eq<='1' when A=B else '0';

gt<='1' when A>B else '0';

lt<='1' when A<B else '0';

end Dataflow;

RTL Diagram:

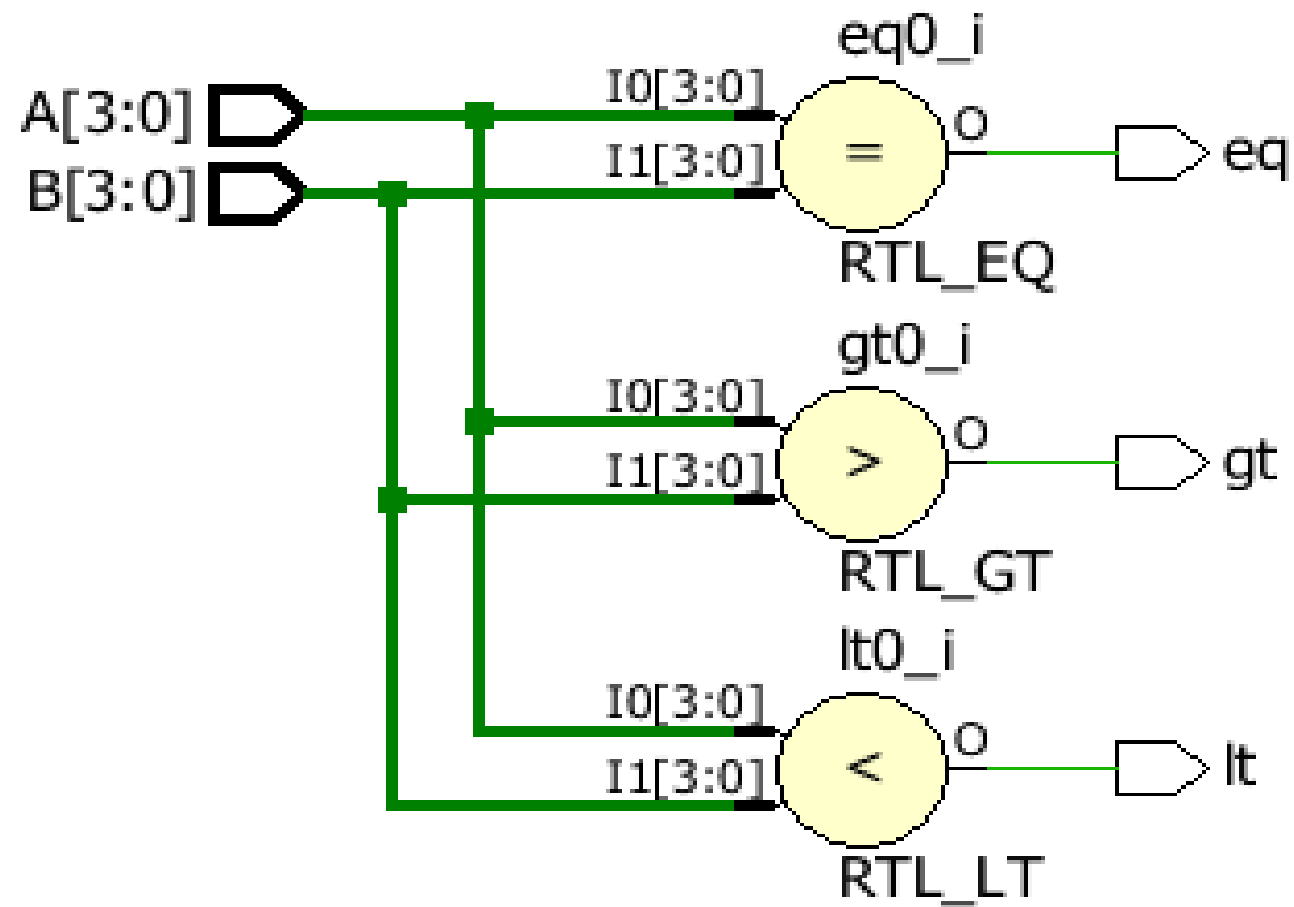

Assignment 3 Day 3

- Design and simulate Data Flow and Behavioural model of
- 2:1 Mux
- 4:1 Mux
- 3:8 Decoder
- Design Dataflow model of 4bits Comparator