

VHDL Lab Day 2

Behavioral Model

AND GATE IN BEHAVIOURAL MODEL

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity and_bv is
```

```
    Port ( a : in STD_LOGIC;
```

```
          b : in STD_LOGIC;
```

```
          c : out STD_LOGIC);
```

```
end and_bv;
```

AND GATE IN BEHAVIOURAL MODEL

architecture Behavioral of and_bv is

begin

 process(a,b)

 begin

 if(a='1')and(b='1')then

 c<='1';

 else

 c<='0';

 end if;

 end process;

end Behavioral;

SIMULATION SOURCE

```
entity and_bv_tb is
--  Port ( );
end and_bv_tb;

architecture Behavioral of and_bv_tb is
component and_bv is
    Port ( a : in STD_LOGIC;
           b : in STD_LOGIC;
           c : out STD_LOGIC);
end component;

signal a1 : STD_LOGIC := '0';
signal b1 : STD_LOGIC := '0';
signal c1 : STD_LOGIC;
```

```
begin
uut: and_df PORT MAP(a=>a1,b=>b1,c=>c1);
    stim_proc: process
    begin
        wait for 100 ns;
        a1<='0';    b1<='1';
        wait for 100 ns;
        a1<='1'; b1<='0';
        wait for 100 ns;
        a1<='1'; b1<='1';
        wait;
    end process;
end Behavioral;
```

OR GATE IN BEHAVIOURAL MODEL

architecture Behavioral of or_bv is

begin

process(a,b)

begin

if(a='1')or(b='1')then

c <='1';

else

c <='0';

end if;

end process;

end Behavioral;

architecture Behavioral of or_bv is

begin

process(A,B)

begin

if(A='0' and B='0')then

C<='0';

else

C<='1';

end if;

end process;

end Behavioral;

COMBINATIONAL CIRCUITS

- **HALF ADDER** : An **adder** is a digital circuit that performs addition of numbers. The **half adder** adds two single binary digits and has two outputs, sum and carry. The carry signal represents an overflow into the next digit of a multi-digit addition.

 


Figure 1: Block diagram of the half adder

A	B	S (sum)	C (carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Table 1: Truth table of the half adder.

HALF ADDER

$$S = \bar{A} \cdot B + A \cdot \bar{B} = A \oplus B$$
$$C = A \cdot B$$

entity ha_df is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

s : out STD_LOGIC;

c : out STD_LOGIC);

end ha_df;

architecture Behavioral of ha_df is

begin

s <= a xor b;

c <= a and b;

end Behavioral;

architecture Behavioral of ha_bv is

begin

process(a,b)

begin

if(a=b)then

s<='0';

else

s<='1';

end if;

if(a='1')and(b='1')then

c<='1';

else

c<='0';

end if;

end process;

end Behavioral;

FULL ADDER :-

- The **full adder** adds three single binary digits and has two outputs - sum and carry.

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

FULL ADDDER

architecture Behavioral of fa_df is

begin

sum <= x xor y xor z;

carry <= (x and y)or(y and z)or (z and x);

end;

architecture Behavioral of full_adder_behavioral is

begin

 process(A,B,C)

 begin

 if(A='0')then

 if(B=C) then

 S<='0';

 else

 S<='1';

 end if;

 if(B='1' and C='1')then

 Cout<='1';

 else

 Cout<='0';

 end if; end if;

 if(A='1')then

 if(B=C)then

 S<='1';

 else

 S<='0';

 end if;

 if(B='0' and C='0')then

 Cout<='0';

 else

 Cout<='1';

 end if;

 end if;

end process;

end Behavioral;

Assignments-2 Day 2

- Design Behavioural models of following logic gates.
- AND,OR,NAND,NOR,XOR,NOT
- Design Data Flow and Behavioural models of Half adder and Full adder