

ALU Model (Behavioral):

VHDL code:

```
use IEEE.NUMERIC_STD.ALL;


entity alu_b is
    Port ( A : in unsigned (3 downto 0);
          B : in unsigned (3 downto 0);
          Ch : in STD_LOGIC_VECTOR (2 downto 0);
          Res : out unsigned (3 downto 0));
end alu_b;

architecture Behavioral of alu_b is

begin
    process(A,B,Ch)
    begin
        case Ch is
            when "000"=>Res<=A+B;
            when "001"=>Res<=A-B;
            when "010"=>Res<=A+1;
            when "011"=>Res<=A-1;
            when "100"=>Res<=A AND B;
            when "101"=>Res<=A OR B;
            when "110"=>Res<=NOT A;
            when "111"=>Res<=A XOR B;
            when others=>NULL;
        end case;
    end process;
end process;
```

end Behavioral;

RTL Diagram:

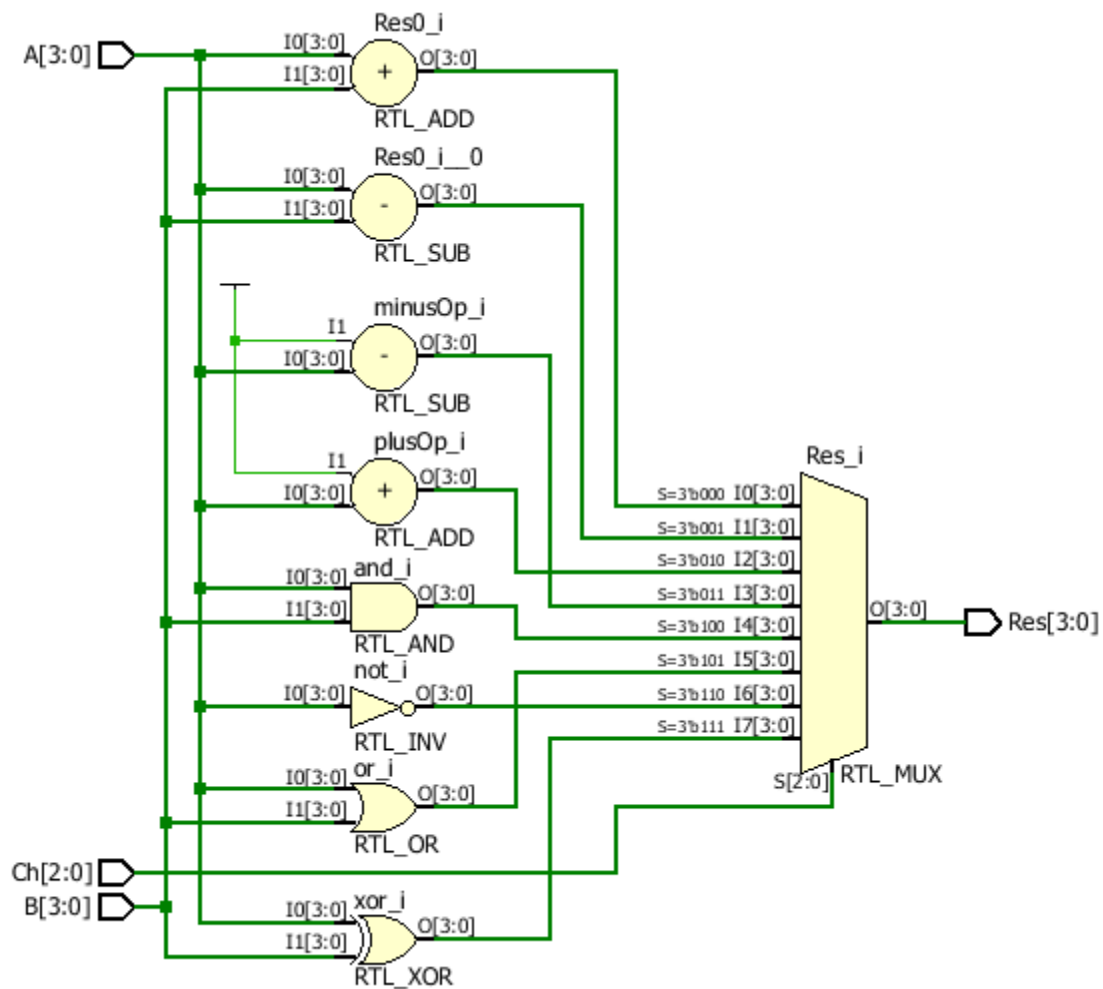

TBW Code:

entity alu_b_tb is

-- Port ();

end alu_b_tb;

architecture Behavioral of alu_b_tb is

component alu_b is

Port (A : in unsigned (3 downto 0);

B : in unsigned (3 downto 0);

```

        Ch : in STD_LOGIC_VECTOR (2 downto 0);

        Res : out unsigned (3 downto 0));

end component;


signal A1 : unsigned (3 downto 0) := "1000";
signal B1 : unsigned (3 downto 0) := "0010";
signal Ch1 : STD_LOGIC_VECTOR (2 downto 0) := "000";
signal Res1 : unsigned (3 downto 0);


begin

    uut: alu_b port map (A=>A1, B=>B1, Ch=>Ch1, Res=>Res1);

    stim_proc: process
    begin
        wait for 100ns;

        Ch1 <= "000";

        wait for 100ns;

        Ch1 <= "001";

        wait for 100ns;

        Ch1 <= "010";

        wait for 100ns;

        Ch1 <= "011";

        wait for 100ns;

        Ch1 <= "100";

        wait for 100ns;

        Ch1 <= "101";

        wait for 100ns;

        Ch1 <= "110";
    end process;
end;

```

wait for 100ns;


Ch1 <= "111";

wait;

end process;

end Behavioral;

Waveform:

 

Full Adder (Structural):

VHDL code:

entity full_adder_structural is

Port (X : in STD_LOGIC;

Y : in STD_LOGIC;

Z : in STD_LOGIC;

Sum : out STD_LOGIC;

```

        Carry : out STD_LOGIC);
end full_adder_structural;

architecture Structural of full_adder_structural is

component half_adder_dataflow is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           S : out STD_LOGIC;
           C : out STD_LOGIC);
end component;

component or_dataflow is
    Port ( X : in STD_LOGIC;
           Y : in STD_LOGIC;
           Z : out STD_LOGIC);
end component;

signal S1: STD_LOGIC;
signal C1: STD_LOGIC;
signal C2: STD_LOGIC;




begin

l1:half_adder_dataflow port map(X,Y,S1,C1);
l2:half_adder_dataflow port map(S1,Z,Sum,C2);
l3:or_dataflow port map(C1,C2,Carry);

```

end Structural;

RTL Diagram:

 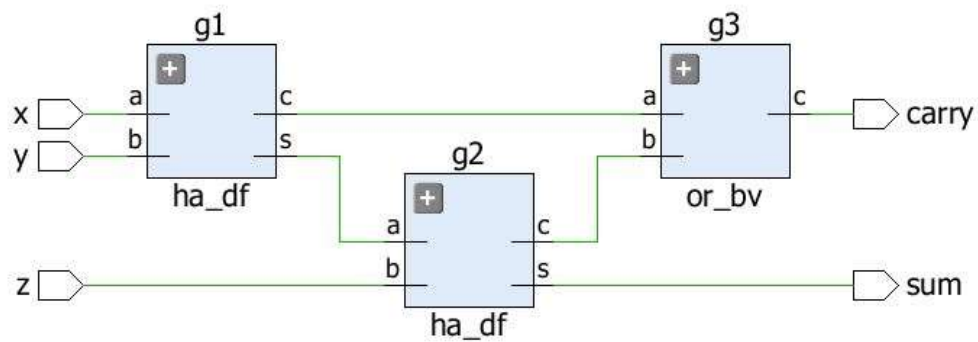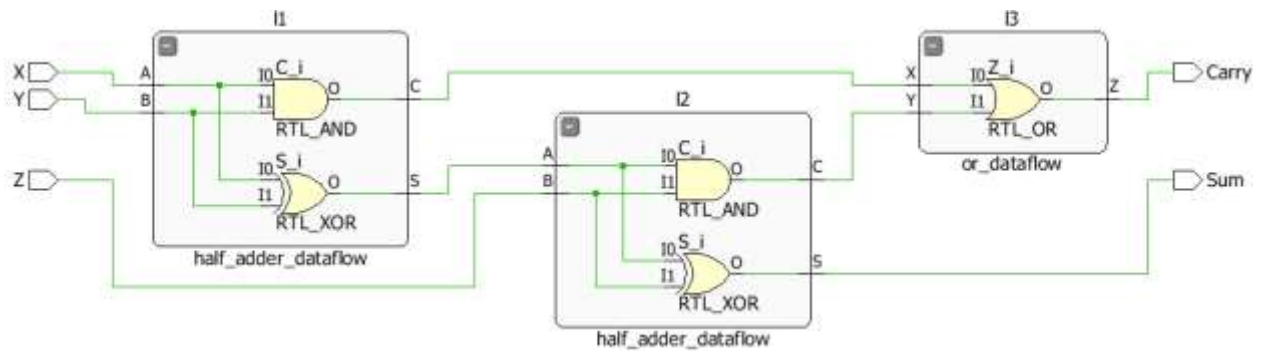

Day 4 Assignment

- 1 Design ALU with 4 logical and 4 arithmetic operations.
- 2 Design Structural model for 8:1 Mux using 4:1 and 2:1 Mux
3. Design Structural model for Full adder using half adder and or gate

Those who are in EDAPlayground

Do Half Subtractor and Full Subtractor along with ALU